

LAB3 GRP7 SESS202 REPORT

VHDL SOURCE CODE 1: TOP LEVEL STRUCTURAL

```
library ieee;
use ieee.std_logic_1164.all;
use ieee.numeric_std.all;

entity LogicalStep_Lab3_top is port (
    clk_in_50      : in      std_logic;
    pb             : in      std_logic_vector(3 downto 0);
    sw             : in      std_logic_vector(7 downto 0); -- The switch inputs
    leds           : out std_logic_vector(7 downto 0); -- for displaying the switch content
    seg7_data      : out std_logic_vector(6 downto 0); -- 7-bit outputs to a 7-segment
    seg7_char1     : out      std_logic; -- seg7
    digi selectors : out      std_logic; -- seg7
    seg7_char2     : out      std_logic; -- seg7
    digi selectors : out      std_logic; -- seg7
);
end LogicalStep_Lab3_top;

architecture Energy_Monitor of LogicalStep_Lab3_top is

-- Components Used
-----
component fourbitcomparator port(

    bitA0, bitA1, bitA2, bitA3, bitB0, bitB1, bitB2, bitB3 : in std_logic;

    AGTB : out std_logic;
    AEQB : out std_logic;
    ALTB : out std_logic

);
end component;

component SevenSegment port ( -- converts a 4-bit number to 7 bit-number to be use for the 7-
segment display
    hex : in std_logic_vector(3 downto 0); -- The 4 bit data to be displayed
    sevenseg : out std_logic_vector(6 downto 0) -- 7-bit outputs to a 7-segment
);
end component;

component segment7_mux port ( -- the mux to turn the 2 7-segment display on simultaneously
    clk : in std_logic := '0';
    DIN2 : in std_logic_vector(6 downto 0);
    DIN1 : in std_logic_vector(6 downto 0);
    DOUT : out std_logic_vector(6 downto 0);
    DIG2 : out std_logic;
    DIG1 : out std_logic
);
end component;

component EnergyControl is port (
    CurrentGreater, CurrentEqual, CurrentSmaller : in std_logic;
    DoorWindowOpenControl : in std_logic_vector(2 downto 0); -- our push buttons
    -- remember it is active low, so 0 means door open
    --Fdoor->pb2 window->pb1 Bdoor ->pb0
    --Fdoor-> led6 window->led5, Bdoor -> led4

    FurnaceON: out std_logic; -- 1 if on
    SystemAtTemp: out std_logic;-- 1 if on
    ACON: out std_logic;-- 1 if on
);
end component;
```

```

        BlowerON: out std_logic;-- 1 if on
        DoorWindowOpenOutput: out std_logic_vector(2 downto 0)-- 1 if on
    );
end component;
-----
signal Current_Temp : std_logic_vector(3 downto 0); -- represents the current Temp
signal Desired_Temp : std_logic_vector(3 downto 0); -- represents the desired temp
signal GT, EQ, LT : std_logic;
signal sevenseg_Current_Temp, sevenseg_Desired_Temp : std_logic_vector(6 downto 0); -- the signal
that goes directly into the sevenseg mux

begin
    ----- input from our switches for temperature -----
    Current_Temp <= sw(7 downto 4); -- left side input
    Desired_Temp <= sw(3 downto 0); -- right side input

    ----- comparing Current_Temp to Desired_Temp -----
    INST1: fourbitcomparator port
    map(Current_Temp(0),Current_Temp(1),Current_Temp(2),Current_Temp(3),
        Desired_Temp(0),Desired_Temp(1),Desired_Temp(2),Desired_Temp(3),
        GT,EQ,LT); -- a bit inefficient in terms of amount if input, but does the job
                    -- could be cleaner

    -----DISPLAYING THE TEMPS-----
    INST2: SevenSegment port map(Current_Temp, sevenseg_Current_Temp);
    INST3: sevenSegment port map(Desired_Temp, sevenseg_Desired_Temp);
    INST4: segment7_mux port map (clk_50, sevenseg_Current_Temp,
    sevenseg_Desired_Temp, seg7_data, seg7_char1, seg7_char2);
    -----END OF DISPLAYING-----

    -----CONTROLLING THE outputs using our Energy Control component-----
    -----
    INST5: EnergyControl port map(GT,EQ,LT, pb(2 downto 0), leds(0), leds(1), leds(2),
    leds(3), leds(6 downto 4) );

    -----
end Energy_Monitor;

```

VHDL SOURCE CODE 2: 1-BIT COMPARATOR

```
library ieee;
use ieee.std_logic_1164.all;
use ieee.numeric_std.all;

entity SingleBitComparator is port (

    bit1    : in std_logic;
    bit2    : in std_logic;

    gt      : out std_logic;
    et      : out std_logic;
    lt      : out std_logic
);

end SingleBitComparator;

architecture Behavioural of SingleBitComparator is

Begin

    gt <= bit1 and not bit2; --bit1 is 1 and bit2 is 0
    et <= NOT (bit1 XOR bit2); --when bit1 and bit2 are the same values
    lt <= not bit1 and bit2; --bit1 is 0 and bit2 is 1

end Behavioural;
```

VHDL SOURCE CODE 3: 4-BITS COMPARATOR

```
library ieee;
use ieee.std_logic_1164.all;
use ieee.numeric_std.all;

entity FourBitComparator is port (

    bitA0, bitA1, bitA2, bitA3, bitB0, bitB1, bitB2, bitB3 : in std_logic;

    AGTB    : out std_logic;
    AEQB    : out std_logic;
    ALTB    : out std_logic

);

end FourBitComparator;

architecture Behavioural of FOurBitComparator is

component SingleBitComparator port(
    bit1    : in std_logic;
    bit2    : in std_logic;

    gt      : out std_logic;
    et      : out std_logic;
    lt      : out std_logic
);

end component;

signal A3LTB3, A3GTB3, A3EQB3, A2LTB2, A2GTB2, A2EQB2, A1LTB1, A1GTB1, A1EQB1, A0LTB0, A0GTB0,
A0EQB0 : std_logic;
signal ALTB_signal , AEQB_signal , AGTB_signal : std_logic;

Begin

    INST1: SingleBitComparator port map(bitA0, bitB0, A0GTB0, A0EQB0, A0LTB0);
    INST2: SingleBitComparator port map(bitA1, bitB1, A1GTB1, A1EQB1, A1LTB1);
    INST3: SingleBitComparator port map(bitA2, bitB2, A2GTB2, A2EQB2, A2LTB2);
    INST4: SingleBitComparator port map(bitA3, bitB3, A3GTB3, A3EQB3, A3LTB3);

    -- equal if all 4 bits compare to equal
    AEQB_signal <= A3EQB3 and A2EQB2 and A1EQB1 and A0EQB0;

    -- greater if all bits compared early are equal and this bit comparing is bigger
    AGTB_signal <= (A3GTB3) or (A3EQB3 and A2GTB2) or (A3EQB3 and A2EQB2 AND A1GTB1) OR
(A3EQB3 AND A2EQB2 AND A1EQB1 AND A0GTB0);

    --else....
    ALTB <= not(AEQB_signal OR AGTB_signal);

    -- just setting the other signal to the real output
    AEQB <= AEQB_signal;
    AGTB <= AGTB_signal;

end Behavioural;
```

VHDL SOURCE CODE 4: ENERGY CONTROL

```
library ieee;
use ieee.std_logic_1164.all;
use ieee.numeric_std.all;

entity EnergyControl is port (
    CurrentGreater, CurrentEqual, CurrentSmaller : in std_logic;
    DoorWindowOpenControl : in std_logic_vector(2 downto 0); -- our push buttons
    -- remember it is active low, so 0 means door open
    FurnaceON: out std_logic; -- 1 if on
    SystemAtTemp: out std_logic;-- 1 if on
    ACON: out std_logic;-- 1 if on
    BlowerON: out std_logic;-- 1 if on
    DoorWindowOpenOutput: out std_logic_vector(2 downto 0)-- 1 if on
);
end EnergyControl;

architecture Behaviour of EnergyControl is

    signal isolatedSystem: std_logic; --- 1 if it is isolated

begin
    -- hooking up the PB to LEDS to show if anything is open
    DoorWindowOpenOutput(0) <= not DoorWindowOpenControl(0);

    DoorWindowOpenOutput(1) <= not DoorWindowOpenControl(1);
    DoorWindowOpenOutput(2) <= not DoorWindowOpenControl(2);

    -- check if everything is shut
    isolatedSystem <= DoorWindowOpenControl(0) AND DoorWindowOpenControl(1) AND
    DoorWindowOpenControl(2);

    -- check if blower should be on
    BlowerON <= (CurrentGreater or CurrentSmaller) AND (isolatedSystem);

    -- check if AC should be on
    ACON <= (CurrentGreater)AND (isolatedSystem);

    -- check if Furnace should be on
    FurnaceON <= (CurrentSmaller) AND (isolatedSystem);


    --check if current temperature is equal
    SystemAtTemp <= (CurrentEqual);

end Behaviour;
```


TABLE1: COMPARATOR TRUTH TABLE

Comparison Inputs from 1-Bit Comparators												4-Bit Comparator Outputs		
A3<B3	A3=B3	A3>B3	A2<B2	A2=B2	A2>B2	A1<B1	A1=B1	A1>B1	A0<B0	A0=B0	A0>B0	A<B	A=B	A>B
0	0	1	X	X	X	X	X	X	X	X	X	0	0	1
1	0	0	X	X	X	X	X	X	X	X	X	1	0	0
0	1	0	0	0	1	X	X	X	X	X	X	0	0	1
0	1	0	1	0	0	X	X	X	X	X	X	1	0	0
0	1	0	0	1	0	0	0	1	X	X	X	0	0	1
0	1	0	0	1	0	1	0	0	X	X	X	1	0	0
0	1	0	0	1	0	0	1	0	0	0	1	0	0	1
0	1	0	0	1	0	0	1	0	1	0	0	1	0	0
0	1	0	0	1	0	0	1	0	0	1	0	0	1	0


GRAPH1: SIMULATION1 where HEXA = 1

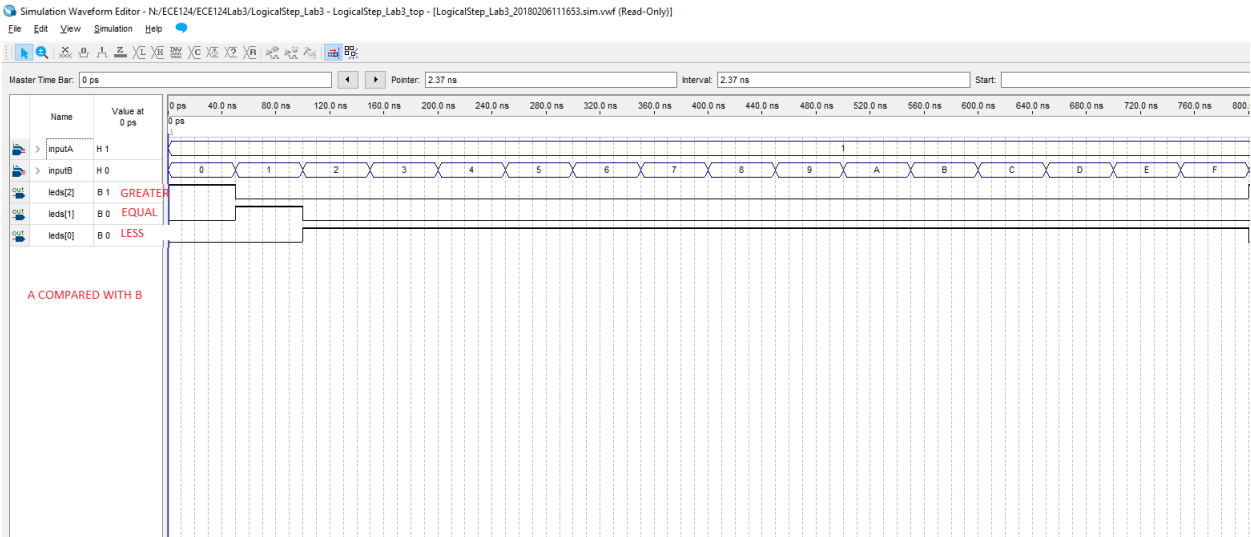


GRAPH2: SIMULATION2 where HEXA = 2

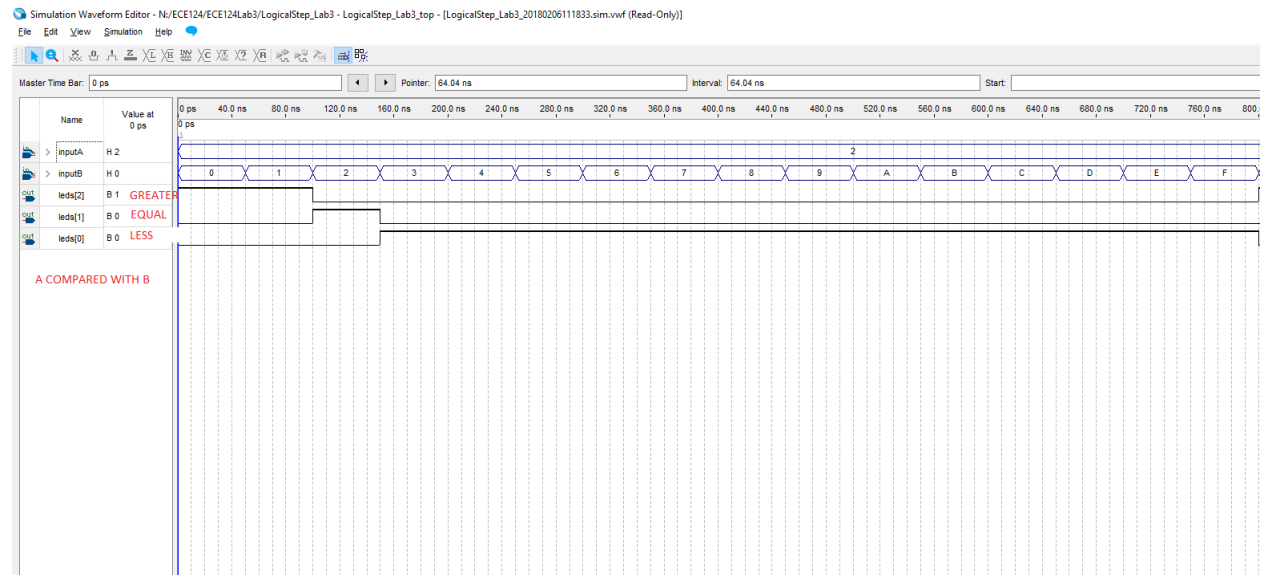


GRAPH3: SIMULATION3 where HEXA = 5

 

GRAPH4: SIMULATION4 where HEXA = 8

 

GRAPH5: RTL OF TOP LEVEL DESGIN

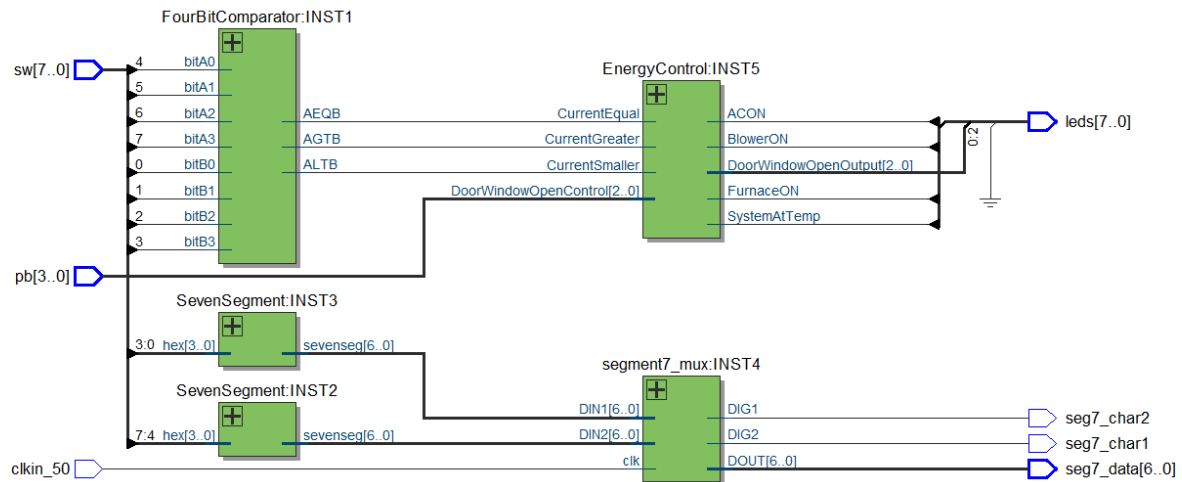

GRAPH6: TOTAL DESIGN LOGIC ELEMENTS

Flow Status	Successful - Sun Mar 04 14:56:21 2018
Quartus Prime Version	15.1.0 Build 185 10/21/2015 SJ Standard Edition
Revision Name	LogicalStep_Lab3_top
Top-level Entity Name	LogicalStep_Lab3_top
Family	MAX 10
Device	10M08SAE144C8G
Timing Models	Final
Total logic elements	43 / 8,064 (< 1 %)
Total combinational functions	43 / 8,064 (< 1 %)
Dedicated logic registers	11 / 8,064 (< 1 %)
Total registers	11
Total pins	30 / 101 (30 %)
Total virtual pins	0
Total memory bits	0 / 387,072 (0 %)
Embedded Multiplier 9-bit elements	0 / 48 (0 %)
Total PLLs	0 / 1 (0 %)
UFM blocks	0 / 1 (0 %)
ADC blocks	0 / 1 (0 %)